

HW #3
CSc 137, Harvey
Adder/Mux (12 pts)

1. Design a Single cell -1 bit Carry propagate (Ripple Carry Adder) full adder. (6 pts)
 - a. Generate the truth table
 - b. Using K-map, determine the logical expression for Carry out (C-out) and Sum (S)
 - c. Based on the logical expression, create the schematic diagram for full adder
2. Design a 1 bit, 2 to 1 multiplexer (Mux). Outputs Y when S = 0; X when S = 1. (6 pts)
 - a. Generate the truth table
 - b. Using K-map, determine the logical expression for output
 - c. Based on the logical expression, create the schematic diagram for Mux

1a.)

Ax	Bx	Cx	Sx	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

R₁
R₂
R₃
R₄
R₅
R₆
R₇
R₈

inputs outputs

1b.)

BCi

A	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Sum

BCi


A	00	01	11	10
0	0	0	1	0
1	0	1	1	1

Cout

$$S_x = ABC + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C$$

$$= A \oplus B \oplus C$$

$$C_{out} = AC + BC + AB$$
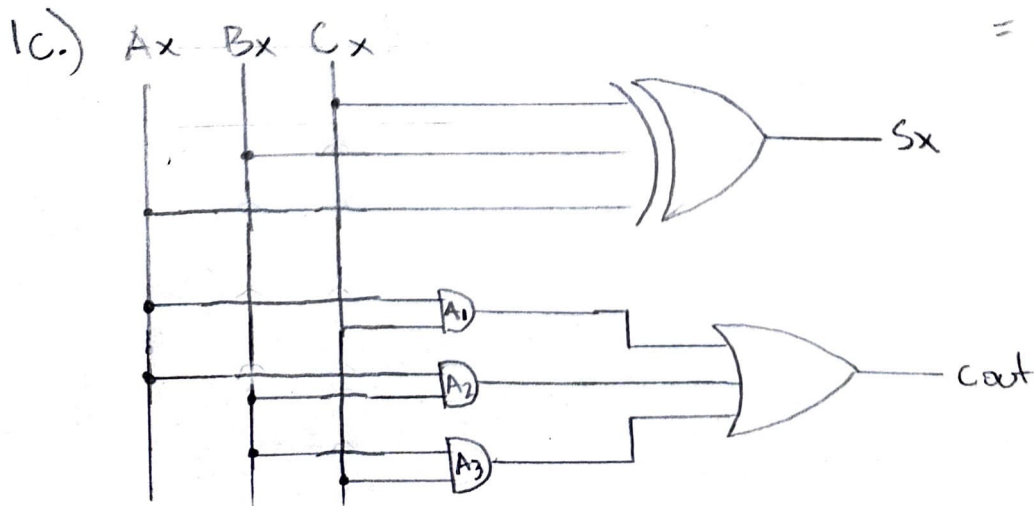
$$= AB + (A \oplus B)C$$


2a.)

S	X	Y	r
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2b.)

	xy	00	01	11	10
R ₁		0	1	1	0
R ₂		0	0	1	1

$$r = \overline{S} \overline{X} Y + \overline{S} X Y + S \overline{X} \overline{Y} + S X Y$$

$$r = S Y + S X$$

2c.)

